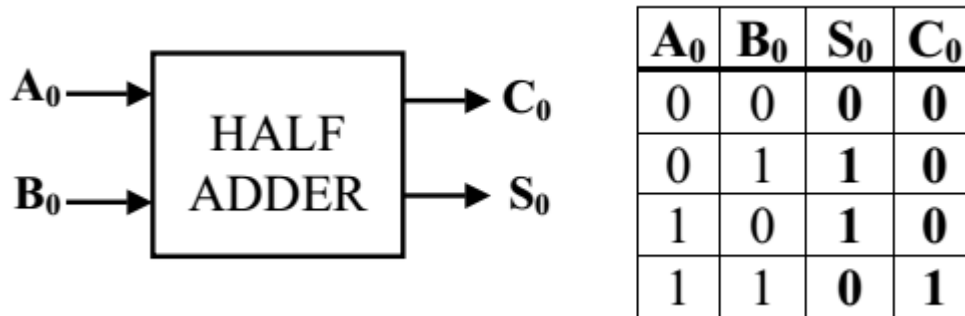


CHAPTER 5: LOGIC CIRCUITS

I. HALF ADDER

The half adder: to add 2 least significant bits (LSB) we do not need a carry input from a previous stage. >> We only need a half adder this will have two inputs A_0 , B_0 and two outputs S_0 and C_0



S_0 : sum out


C_0 : carry out

The **logic** equations are:

$$S_0 = \overline{A_0}B_0 + A_0\overline{B_0} = A \oplus B > (XOR \text{ Gate})$$

$$C_0 = A_0B_0 > (AND \text{ Gate})$$

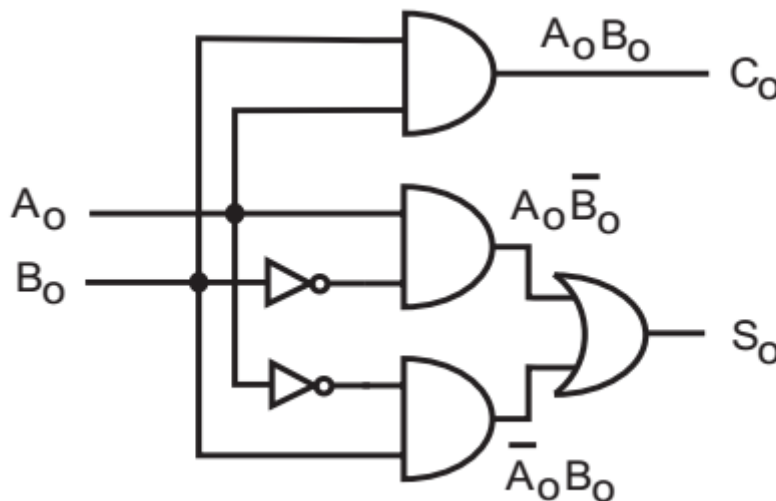The **logic diagram** can also be expressed as follows:



II. FULL ADDER

a. Using normal method

For all other bits (except the LSB) a half adder **will not** suffice because there **may be a carry input** from a previous stage.

A full adder has **3 inputs**: A_K , B_K , C_{K-1} AND **2 OUTPUTS**: S_K , C_K C_{K-1} = carry in from the **previous** stage C_K = carry out to the **next** stage



A_k	B_k	C_{k-1}	S_k	C_k
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

The **logic** equations are:

$$S_K = \bar{A}_K \bar{B}_K C_{K-1} + \bar{A}_K B_K \bar{C}_{K-1} + A_K \bar{B}_K \bar{C}_{K-1} + A_K B_K C_{K-1}$$

$$C_K = \bar{A}_K B_K C_{K-1} + A_K \bar{B}_K C_{K-1} + A_K B_K C_{K-1} + A_K B_K \bar{C}_{K-1}$$

K-MAP FOR S_K :

		$A_K B_K$			
		0 0	0 1	1 1	1 0
C_{K-1}	0	0	1	0	1
	1	1	0	1	0


No simplification possible

k-map for C_K

$A_K B_K$					
C_{K-1}		0 0	0 1	1 1	1 0
	0	0	0		0
	1	0			


$$C_K = B_K C_{K-1} + A_K C_{K-1} + A_K B_K$$

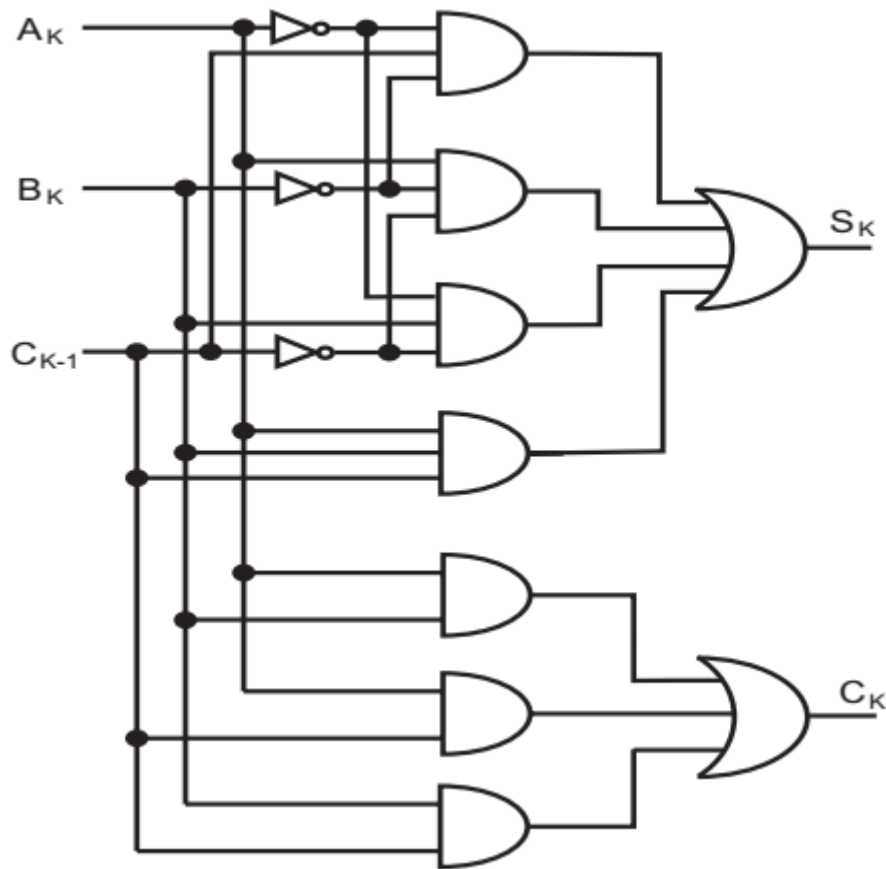The **logic** diagram for a **full adder** is:



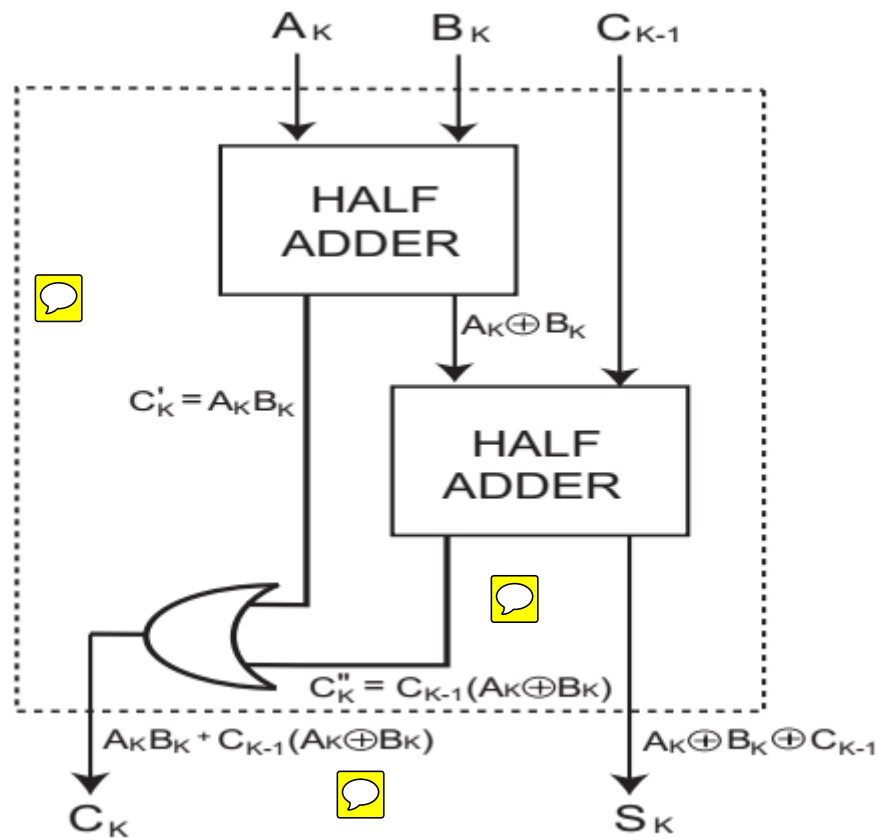b. Full adder using half adders

One half adder adds A_K to B_K to give an intermediate sum S'_K and carry C'_K .
 Another half adder adds S'_K and C_{K-1} to give the final sum S_K and another intermediate carry C''_K .
 there will be a final carry if either C'_K or C''_K are "1"



Remember the Boolean operation for half adder:

$$S'_K = A_K \oplus B_K$$

$$C'_K = A_K B_K$$

For full adder:

$$S_K = A_K \oplus B_K \oplus C_{K-1}$$

$$C_K = A_K B_K + C_{K-1}(A_K \oplus B_K)$$

PROOF:


$$\begin{aligned} S_K &= \bar{A}_K \bar{B}_K C_{K-1} + \bar{A}_K B_K \bar{C}_{K-1} + A_K \bar{B}_K \bar{C}_{K-1} + A_K B_K C_{K-1} \\ &= C_{K-1}(\bar{A}_K \bar{B}_K + A_K B_K) + \bar{C}_{K-1}(\bar{A}_K B_K + A_K \bar{B}_K) \\ &= C_{K-1}(A_K \oplus B_K) + \bar{C}_{K-1}(A_K \oplus B_K) \\ &= A_K \oplus B_K \oplus C_{K-1} \end{aligned}$$

$$\begin{aligned} C_K &= \bar{A}_K B_K C_{K-1} + A_K \bar{B}_K C_{K-1} + A_K B_K \bar{C}_{K-1} + A_K B_K C_{K-1} \\ &= A_K B_K (C_{K-1} + \bar{C}_{K-1}) + C_{K-1}(\bar{A}_K B_K + A_K \bar{B}_K) \\ &= A_K B_K + C_{K-1}(A_K \oplus B_K) \end{aligned}$$

III. THE PARALLEL ADDER:

Also called ripple carry adder used to add **two n-bit** numbers. it consists of n full adders where the carry output of each stage is the carry in of the next stage.

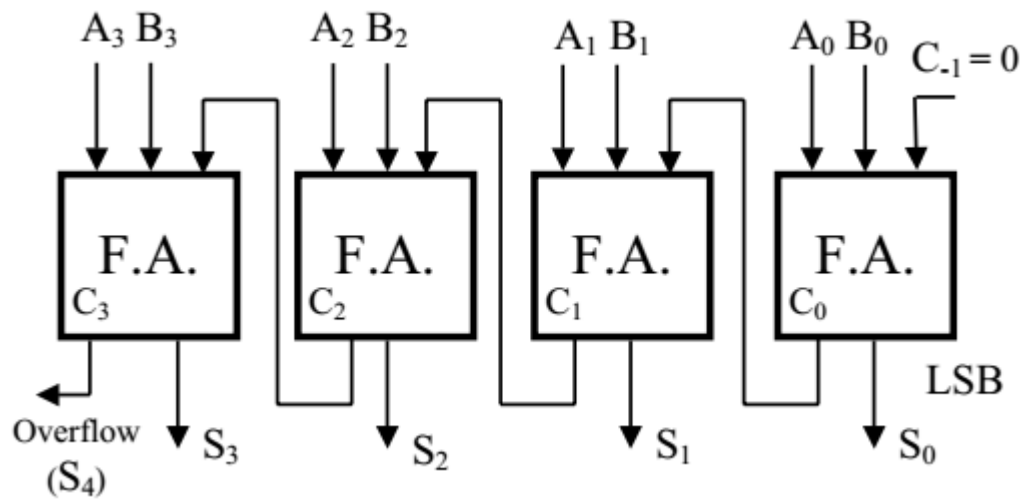Example: 4-bit parallel adder add $A_3A_2A_1A_0$ AND $B_3B_2B_1B_0$



$C_3 = 1 \gg \gg$ over flow

E.G. $A = \mathbf{1010} \quad (10_{10})$
 $B = \mathbf{1001} \quad (9_{10})$
 Overflow $\leftarrow (1)0011 \rightarrow 3_{10}$